

CSE350

DIGITAL ELECTRONICS AND PULSE TECHNIQUES

Lab- 04



Inspiring Excellence


Name: MD. Abdul Kahhar Siddiki Shan

ID: 18301221


Section- 02

Date of Submission- 2 August,2021

Binary-weighted register

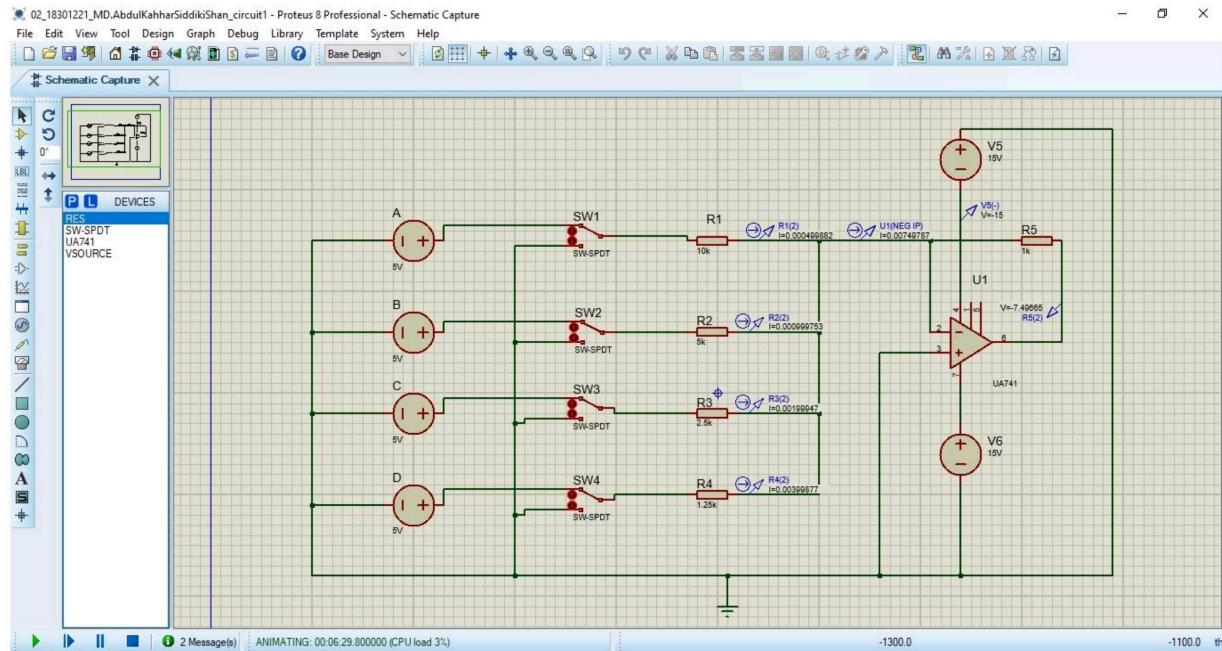

R and 2R Register

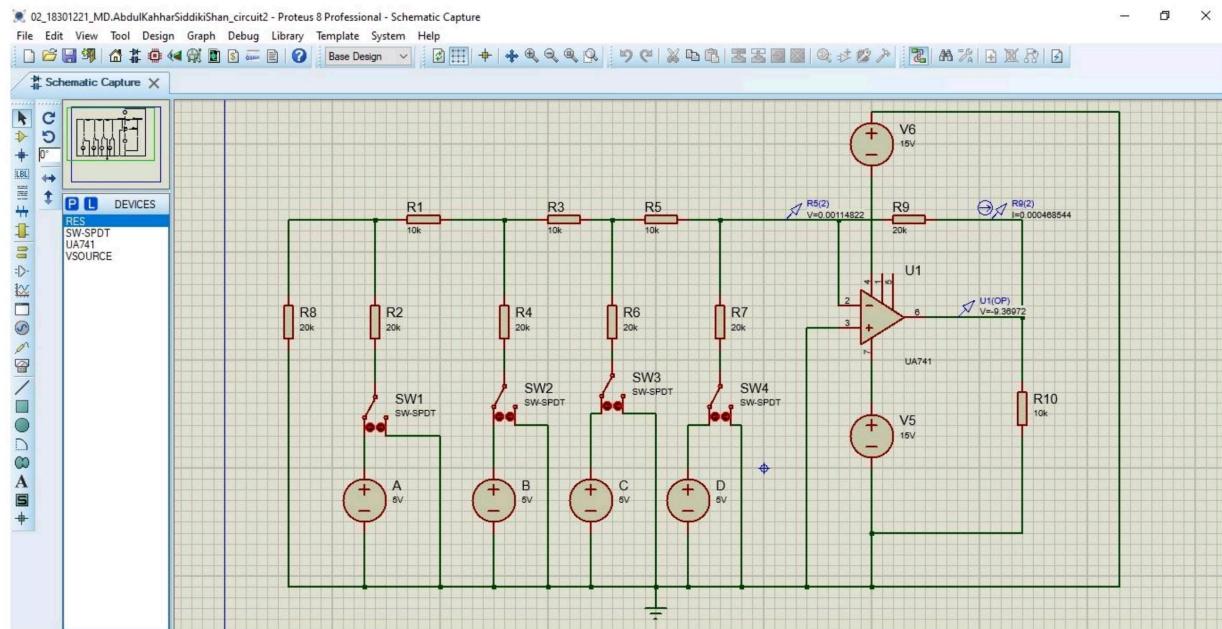

18301221

Datasheet for circuit-1

Input Configuration	D	C	B	A	Output Voltage
1	0	0	0	0	0.002722
2	0	0	0	5	-0.4972
3	0	0	5	0	-0.99
4	0	0	5	5	-1.49
5	0	5	0	0	-1.99
6	0	5	0	5	-2.49
7	0	5	5	0	-2.99
8	0	5	5	5	-3.49
9	5	0	0	0	-3.99
10	5	0	0	5	-4.49
11	5	0	5	0	-4.99
12	5	0	5	5	-5.49
13	5	5	0	0	-5.99
14	5	5	0	5	-6.49
15	5	5	5	0	-6.99
16	5	5	5	5	-7.49

18301221

2
Data sheet for circuit -2

Input Configuration	D	C	B	A	Output Voltage, V _O (V)
1	0	0	0	0	0.00495909
2	0	0	0	5	-0.62
3	0	0	5	0	-1.245
4	0	0	5	5	-1.869
5	0	5	0	0	-2.49
6	0	5	0	5	-3.119
7	0	5	5	0	-3.74
8	0	5	5	5	-4.3699
9	5	0	0	0	-4.99
10	5	0	0	5	-5.619
11	5	0	5	0	-6.24
12	5	0	5	5	-6.86
13	5	5	0	0	-7.49
14	5	5	0	5	-8.119
15	5	5	5	0	-8.749
16	5	5	5	5	-9.369


18301221

Report:

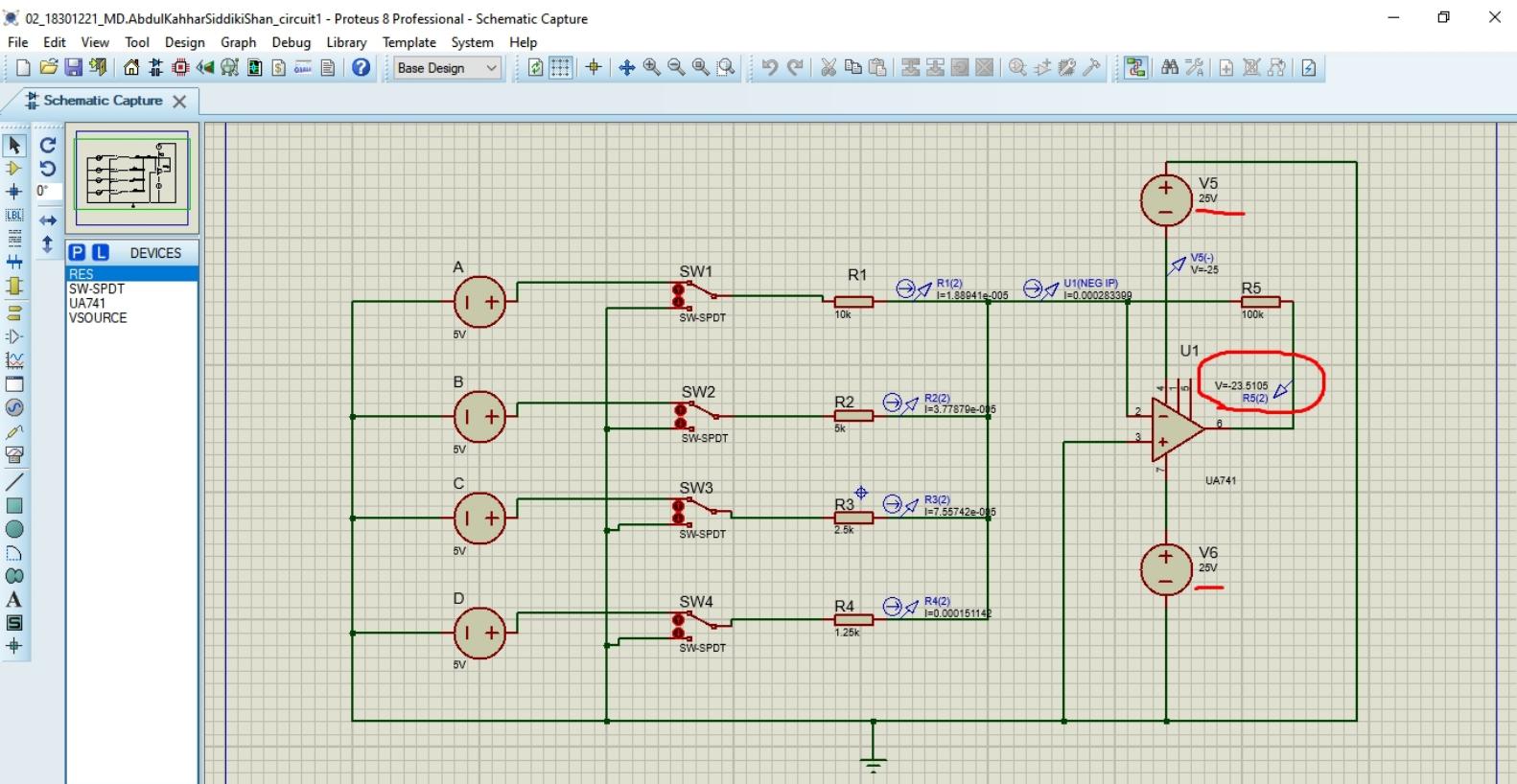1. Can you get output higher than 15v in D2A converters?

If so, how?

→ Yes, i can get output higher than 15V in D2A converter. To get it, i have to increase the value of RF resistor. That will not be enough. I have to increase the input voltage of amplifier which added in 4 and 7 pin. If we increase that voltage, the output voltage will be more than 15V.



2. What is the full step output and resolution for both D2A converters.

→ Full step output for both D2A are:

$$\text{Binary-Weighted Register} \rightarrow \{(16-1) \times 0.5\} = 8.5 \text{ V}$$

$$\text{For } R \text{ and } 2R \rightarrow \{(16-1) \times 0.62\} = 9.3 \text{ V}$$

Resolution stands for changing output.

$$\text{Resolution} = \frac{R_f}{R_A} V_{\text{High}}$$

$$= \frac{1}{10} \times 5$$
$$= 0.5$$

Resolution for Binary-weighted

$$\text{resistor} = 0.5$$

$$\text{Resolution for } R2R = 0.62$$

3. Explain how you get the analogue output voltage of R2R D2A converters? Select one data entry and validate the data with necessary circuits and calculation.

$$V_o = -R_f \left(\frac{1}{R_1} \times V_A + \frac{1}{R_2} \times V_B + \frac{1}{R_3} \times V_C + \left(\frac{1}{R_4} \times V_D \right) \right)$$

$$\text{Let, } V_A = 5, V_B = V_C = V_D = 0$$

$$V_o = -R_f \left(\frac{1}{10} \times 5 + \left(\frac{1}{10} \times 0 \right) + \left(\frac{1}{10} \times 0 \right) + \left(\frac{1}{10} \times 0 \right) \right)$$

$$= -0.5$$

In the circuit calculation in Proteus we got $0.49 \approx 0.5$. So, the data is validate

for R2R:

$$V_{out} = \frac{V_A + 2V_B + 4V_C + 8V_D}{2^n}$$

$$V_{out} = - \left(\frac{V_{ref} \times R_f}{R} \right) \sum_{i=0}^{n-1} \frac{B_i}{n^{n-i}}$$

$$\Rightarrow V_{out} = - \frac{2R_f}{R_f} \left(\frac{V_A}{2^4} + \frac{V_B}{2^3} + \frac{V_C}{2^2} + \frac{V_D}{2^1} \right)$$

18301221

5


When, ~~$A = \infty$~~

$$V_A = 5V, V_B = V_C = V_D = 0$$

$$\therefore V_{out} = -\frac{5 \times 2}{1} \times 1$$

$$V_{out} = -2 \left(\frac{5}{16} + 0 + 0 + 0 \right)$$
$$= -0.625V$$

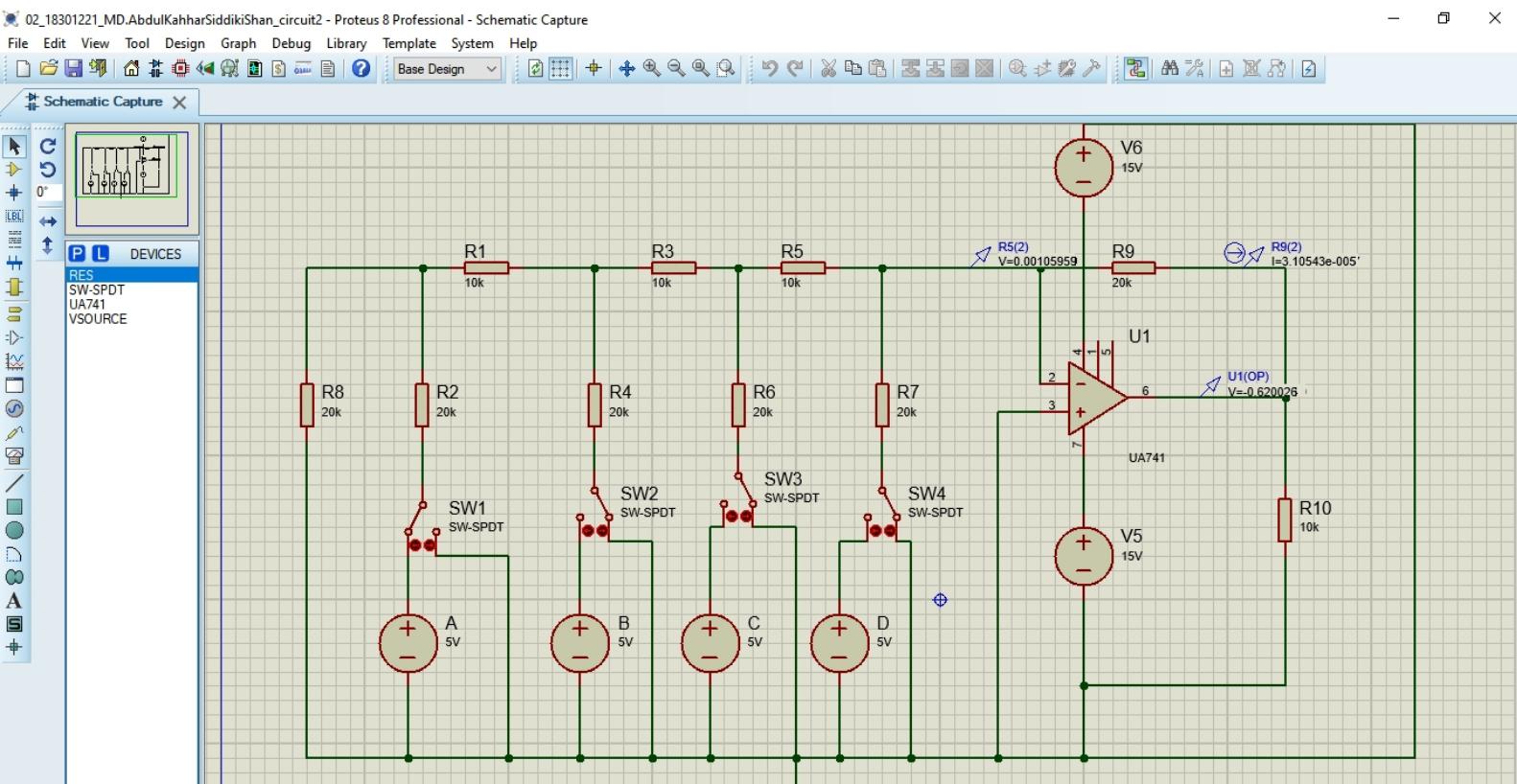This value matches with picotest's value
which I will provide am providing below:



4. What will be the analog output for the above circuit
 (you can either of D2A converter) if the high input voltage
 is the sum of last two digit of your students ID number
 and the low input is zero? Draw a table and fill up it
 for all possible combination

→ My ID = 18301221

$$\text{Last two digit} = 21, \text{Sum} = 2 + 1 = 3V$$

Input Configuration	D	C	B	A	Output Voltage $V_o(V)$
1	0	0	0	0	0.0027
2	0	0	0	3	-0.297
3	0	0	3	0	-0.59
4	0	0	3	3	-0.89
5	0	3	0	0	-1.19
6	0	3	0	3	-1.49
7	0	3	3	0	-1.79
8	0	3	3	3	-2.09216
9	3	0	0	0	-2.39
10	3	0	0	3	-2.69
11	3	0	3	0	-2.99
12	3	0	3	3	-3.29
13	3	3	0	0	-3.59
14	3	3	0	3	-3.89
15	3	3	3	0	-4.19
16	3	3	3	3	-4.49

2


18301201

5. How does the step size vary with respect to RF (feedback register).

$$\text{Hence, current} = \frac{0 - V_o}{R_f}$$

If the value of R_f increases, the V_o will increase. So, if R_f changes step size will change. [Taking 0.49 as 0.5
0.99 or 1]

Graph for circuit-1

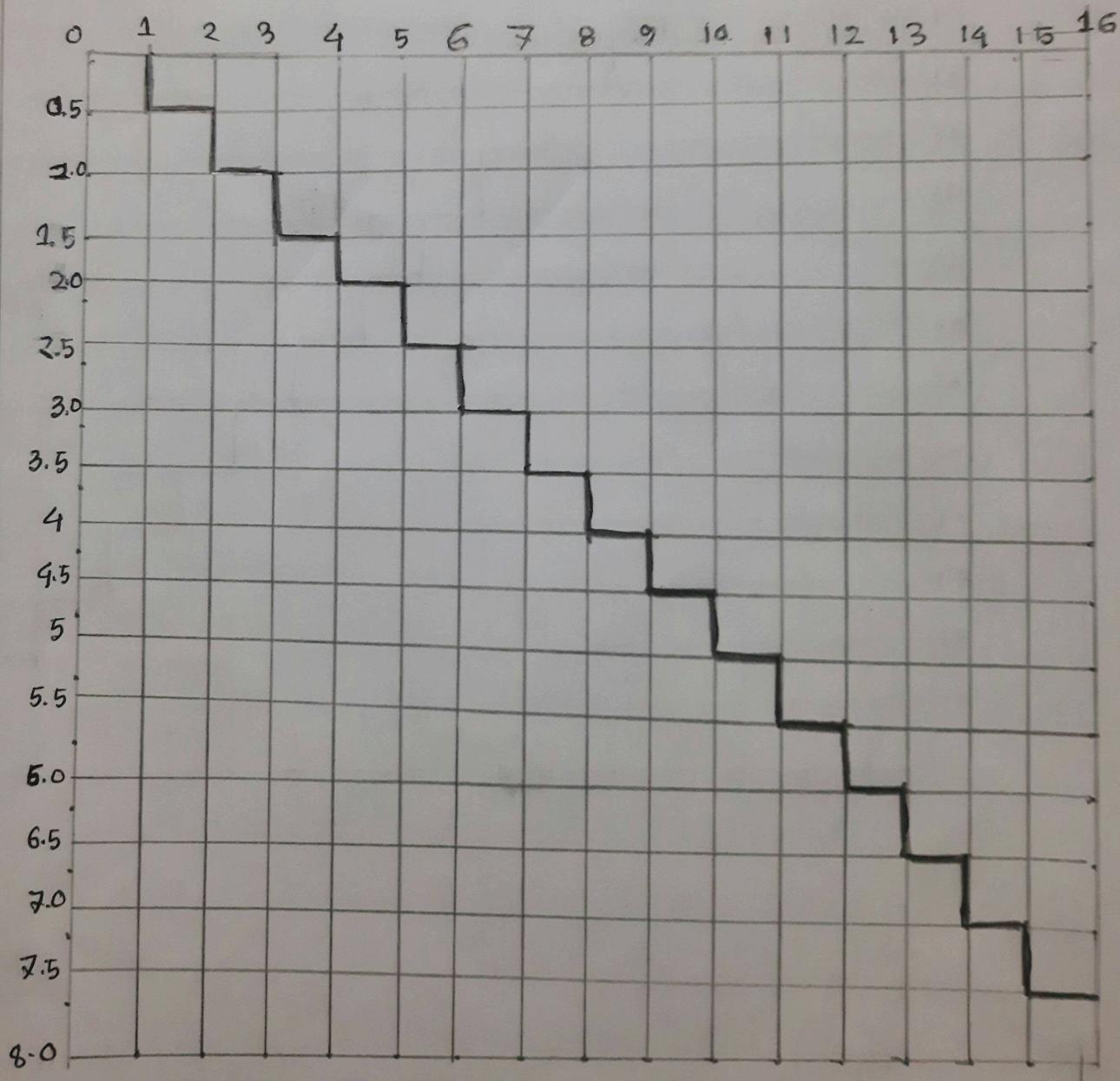

8

18301221

Graph for circuit - 2

