

CSE350

DIGITAL ELECTRONICS AND PULSE TECHNIQUES

Lab- 02




Name: MD. Abdul Kahher Siddiki Shan

ID: 18301221

Section- 02

Date of Submission- 10 July,2021

Circuit diagram of NAND gate:

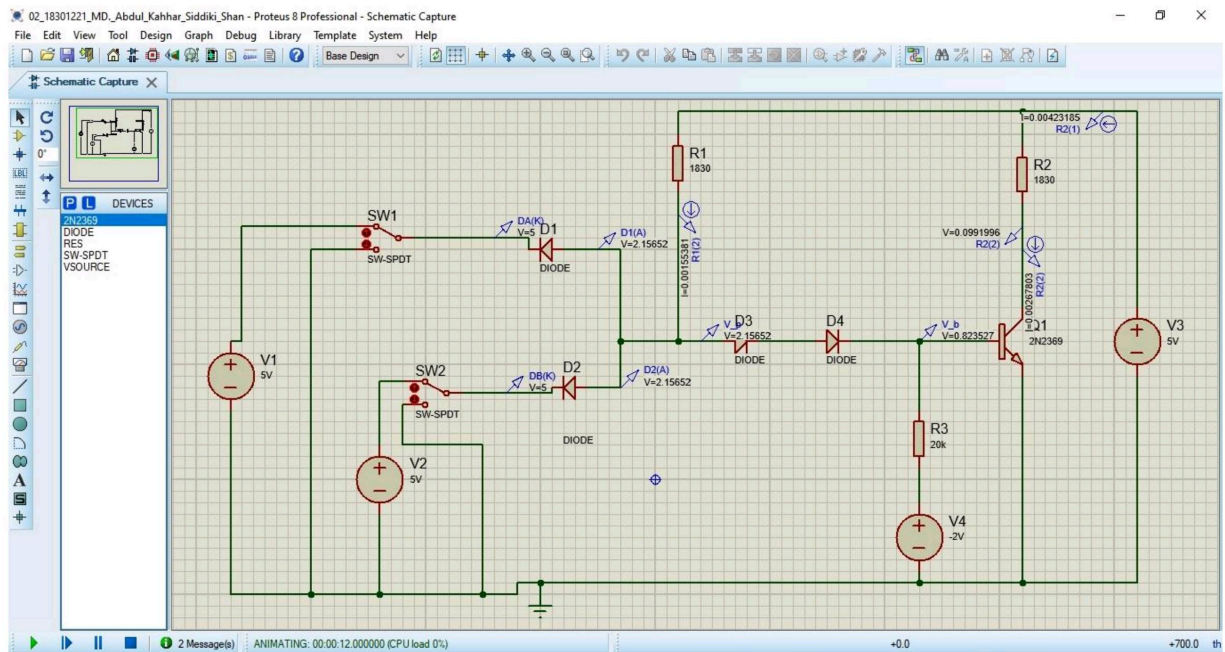

3.


Input _A	Input _B	V_{DA}	V_{DB}	V_p	I_{R1}	I_{R2}	V_b	Output _Y
0	0	0.6586	0.6586	0.6586	0.00237	$1.7236e^{-01}$	-0.516	5
0	1	0.6765	-4.3232	0.6767	0.0023	$1.722e^{-11}$	-0.499	5
1	0	-4.3232	0.6765	0.6767	0.0023	$1.722e^{-011}$	-0.499	5
1	1	-2.8434	-2.8434	2.1565	0.001553	0.002678	0.8235	0.0992

4.

Input _A	Input _B	V_p	V_b	Output _Y
1	0	0.676729	-0.499	5
1	1	2.1565	0.823528	0.09919

Report

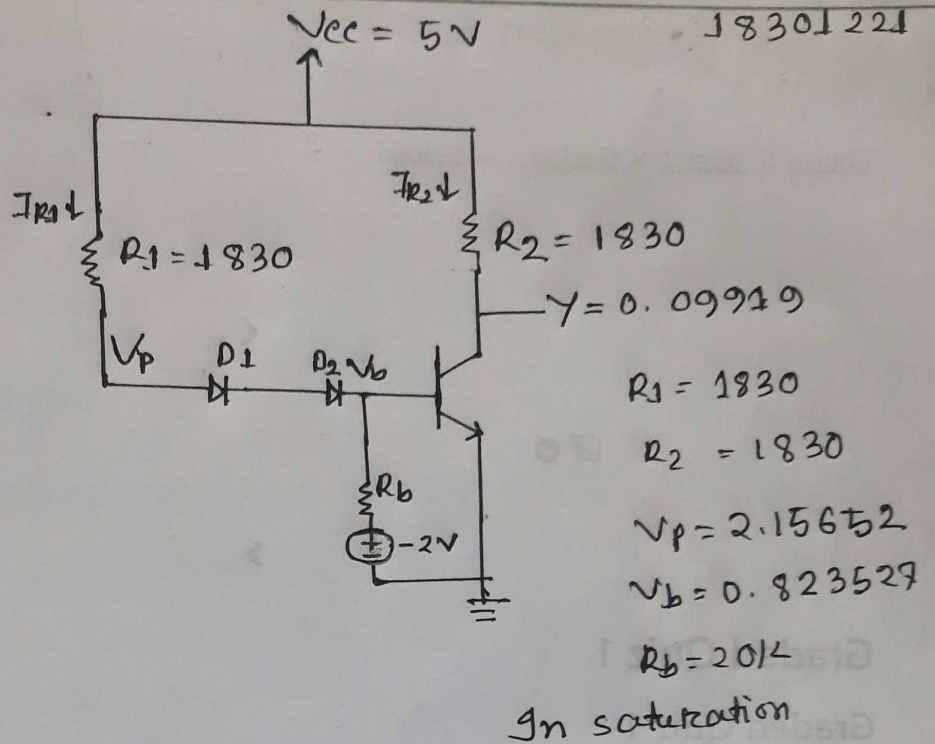- Assume that Logic High has been applied to both inputs of the circuit shown in fig: 1. Draw the partial circuit consisting of only those components which remain active.



2. Explain the logic operation in the table 2 (Laboratory task step 4) How did you reach that logic operation from NAND operation of figure 1.

→ In table-4, we can see that, when the input is low, the output is high. When the input is high, the output is low. which is the behaviour of an inverter. In inverter when we provide low input, it will give high output and while input high, the output is low. so, while input A constant and we are changing the input value of B, the

circuit is working as an inverter.

3. Explain briefly how NAND operation is performed in the circuit.

→ NAND gate made with two gates and they are AND gate, not gate. Actually it provides the reverse output of AND gate. Describing it with example below:

Case-01:

Input $A=0$, Input $B=0$:

Here when the both inputs are low, diodes D_1 and D_2 are turned on and current will flow through it. The voltage of $V_p = 0.65588V$, which is not enough to activate diode D_3 and D_4 as anode voltage of D_3 is less than cathode voltage of D_3 . So, D_3 and D_4 will be open circuit. So, transistor will be in cut off mode. So, there will be no current through the transistor. So, the output voltage will be equal to V_{cc} and output voltage is high.

Case-02:

Input $A=0$, Input $B=1$

As one input is high, it will create open circuit in diode D_1 . But, other one is low and diode D_2 will be on, current will flow through it. V_p voltage will not be enough to activate the diode D_3 and D_4 . So, they will be on open circuit. The transistor will be in cut off mode. So, the output voltage will be high.

case-03:

Input $A=1$, Input $B=0$

It will work same as case-02. only D_1 will be active and D_2 will be open circuit. D_3 and D_4 will be open circuit. ~~Trans~~ as V_p is low. Transistor will be in cut off mode. High output will generate in output.

Case-04:

Input $A=1$, Input $B=1$:

As both inputs are high, the diode D_1 and D_2 will be on Open circuit as their cathode voltage is higher than anode voltage. But, the voltage of V_p will be enough to turn on diode D_3 and D_4 . As a result the transistor

4. will work. Actually, the transistor is working on saturation mode. In addition, we get lower output in the output voltage which is 0.0919 V .

To sum up, in the above mentioned way, the NAND operation performed in the circuit.

4. Using products data, Find the operation mode of A_1 when one of the inputs is High and other one is low.

→ From the proteus data, while one input is high and another input is low, the transistor operation is cut off mode. Here, $I_B = I_C = I_E = 0$ which is the characteristic of cut off mode. The output voltage is also High.

$$\text{Here, } V_E > V_B$$

$$V_C > V_B$$

$$I_B = I_C = I_E = 0$$

So, it is in cut off (verified)

5. What is the maximum value of inputs A, B to keep the output High? (Use simulation data)

→ After analysing the simulation data i found that the maximum value of inputs A, B to keep the output high is $4.2V$. Below i will show the screen shot of that simulation data.

